

Electronics 101

2011-09-07, FIXME, Lausanne


Content

- Seeeduino/Arduino presentation
- Voltage, Current, Resistors : Ohm's law
- Components: Switch, LED, Digital I/O
- Practice: Blink a LED (with the Switch)
- Circuit: Voltage divider
- Components: Potentiometer, Analog input, Servo
- Practice: Drive the servo with Potentiometer
- Components: Resistor sensors (Thermistor, photo resistor)
- Practice: Drive the servo with resistor sensors

- Bonus time (Capacitor, PWM - Analog output, Buzzer)


Seeeduino/Arduino

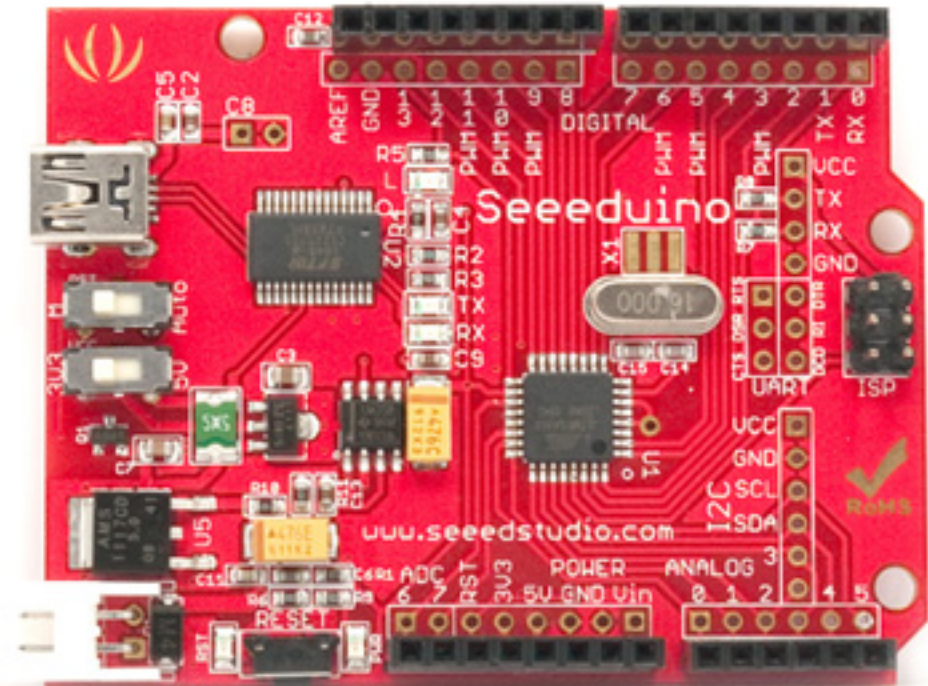- Open source
- Important community
- Shields





Ohm's law

- $V = R I$

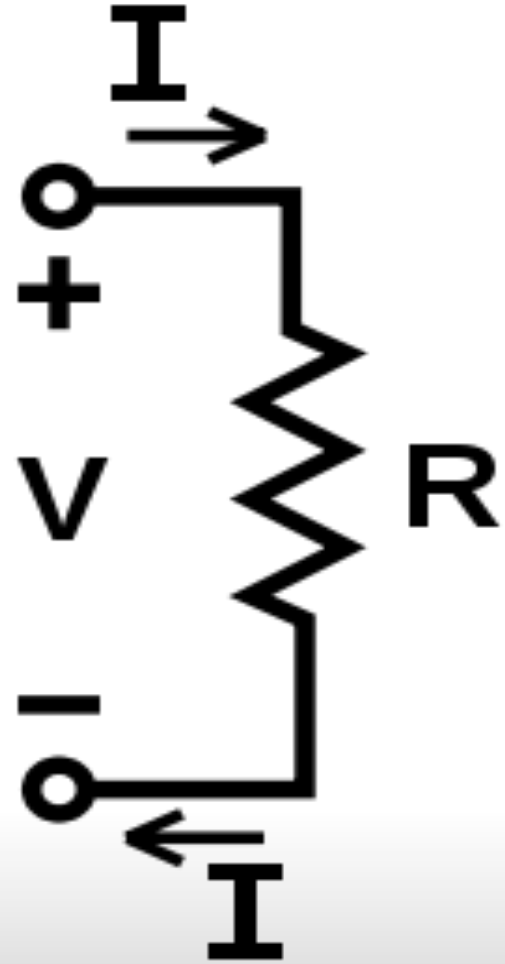







Resistor

Limits current according to Ohm's law

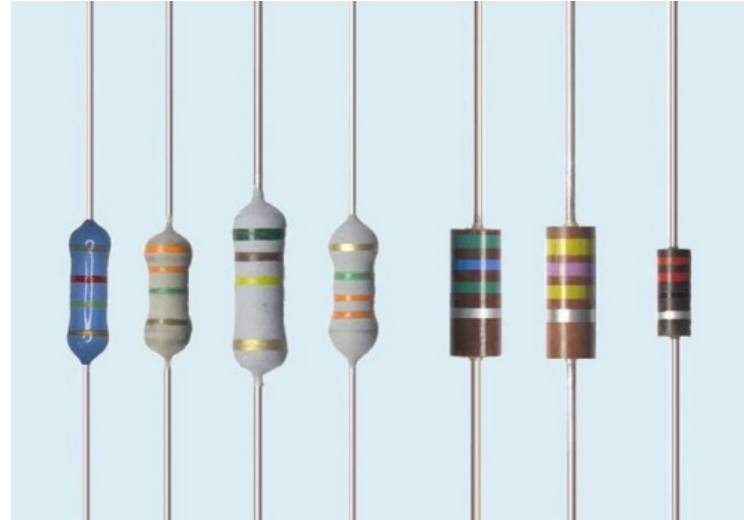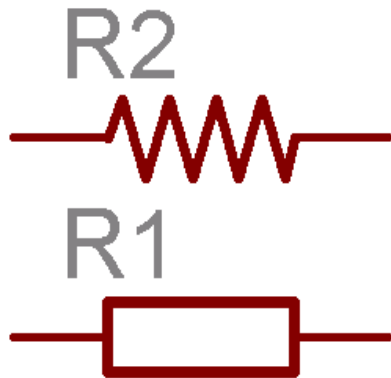

Switch




Allows or not the current to flow

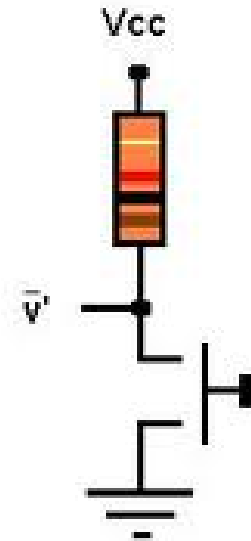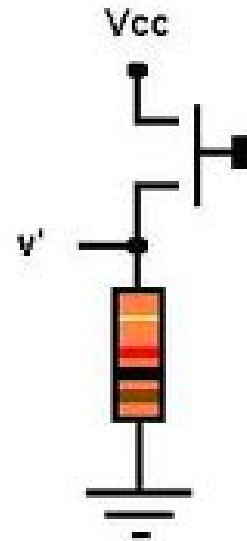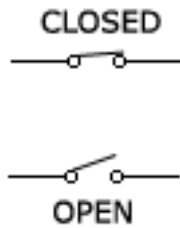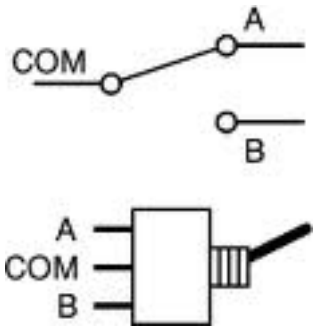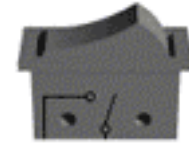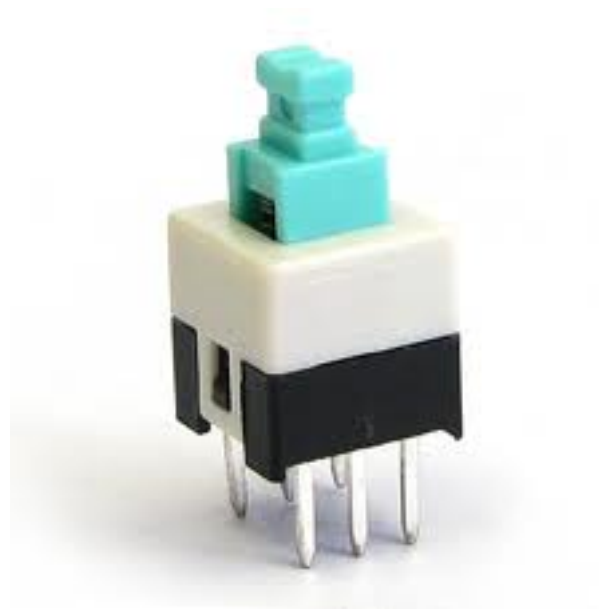

Diode and LED



Allows current only in one direction

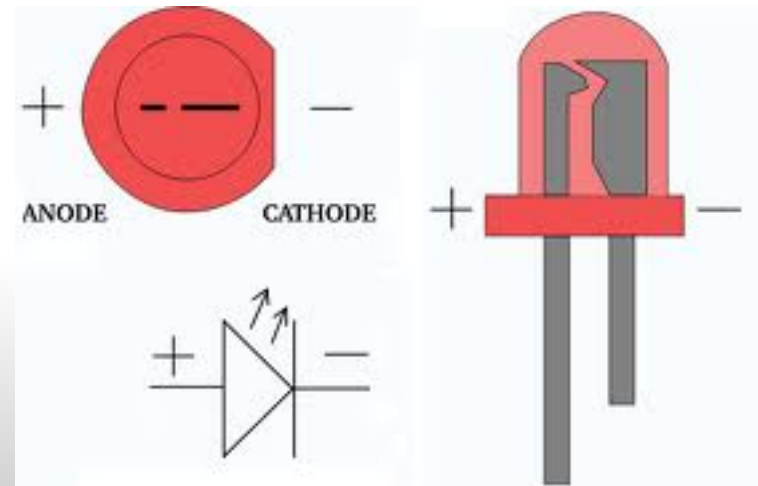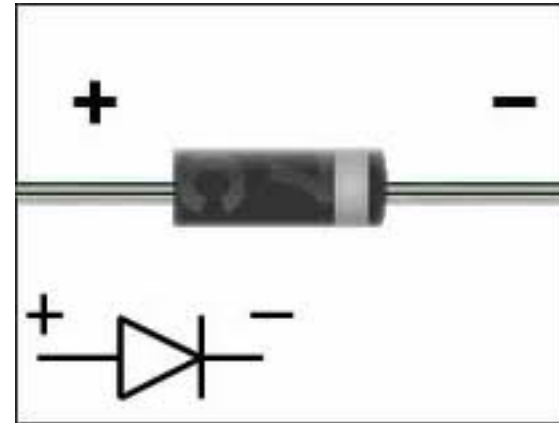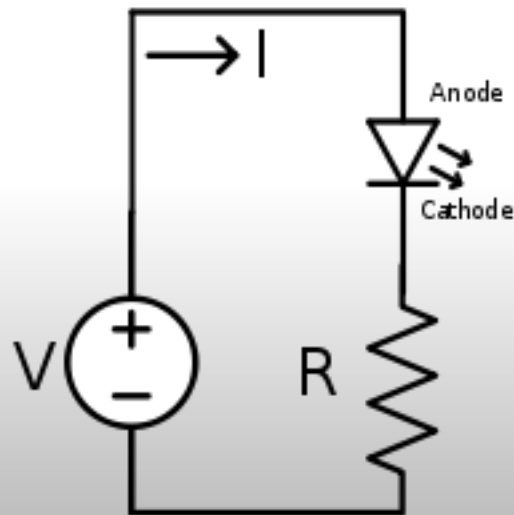- Diodes: $V_f = 0.7V$
- LED:
 - $V_f = [1.8; 3.3]V$
 - Current: $[10; 25] \text{ mA}$



Digital Input/Output

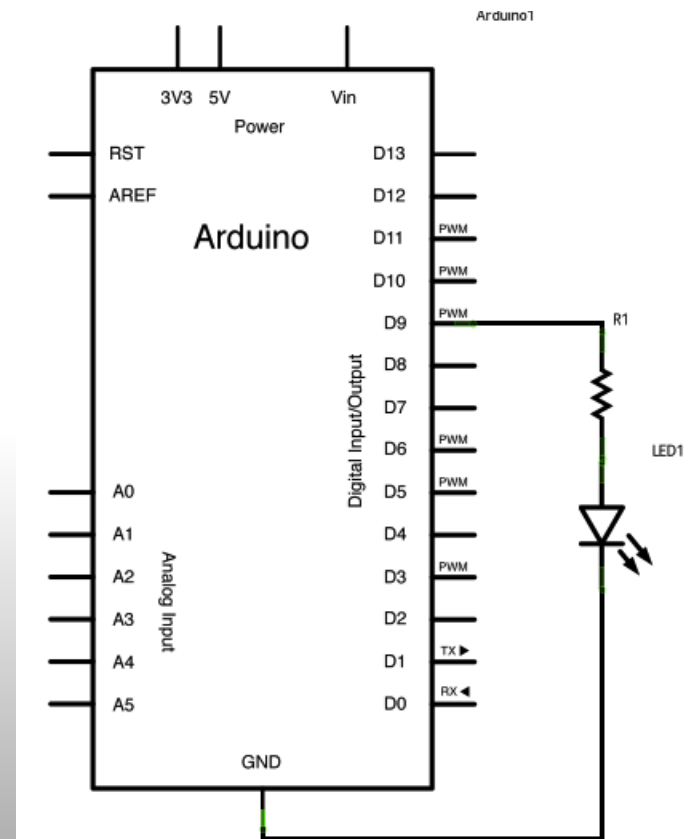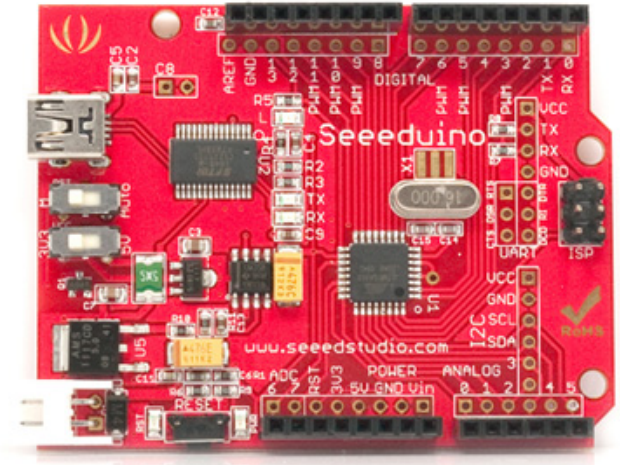- Output:
 - 1 -> 5V
 - 0 -> 0V
 - Current up to 25 mA
- Input:
 - [0; 1.5V] -> 0
 - [3.5V; 5V] -> 1
 - Between the two -> ???
 - No current flows in




Practice

- Blink LED : <http://arduino.cc/en/Tutorial/Blink>
- Switch : <http://arduino.cc/en/Tutorial/DigitalReadSerial>
- Try to understand the schematics and why they choose those values (you will have to change one value)

Voltage divider


- One of the way to divide a voltage
- Only valid if no current flows through V_{out}
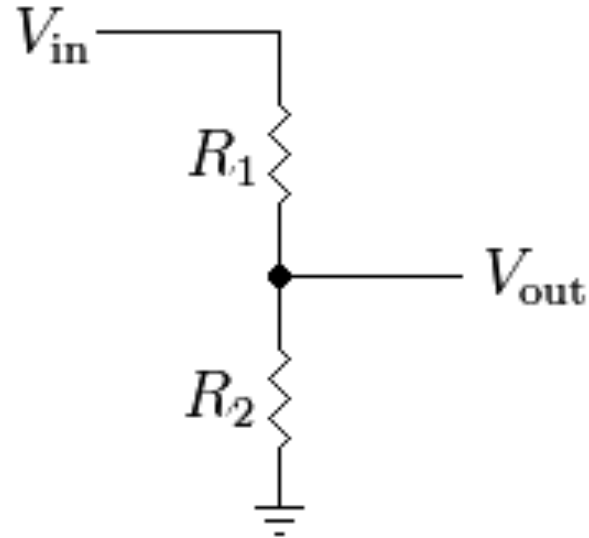
$$V_{out} = \frac{R_2}{R_1 + R_2} \cdot V_{in}$$





Potentiometer

- Is a variable Voltage Divider

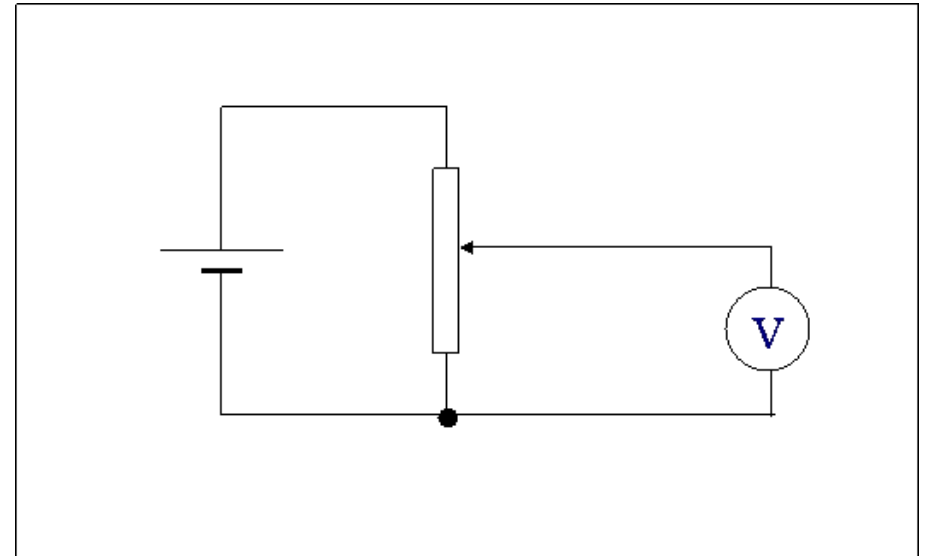




Analog input

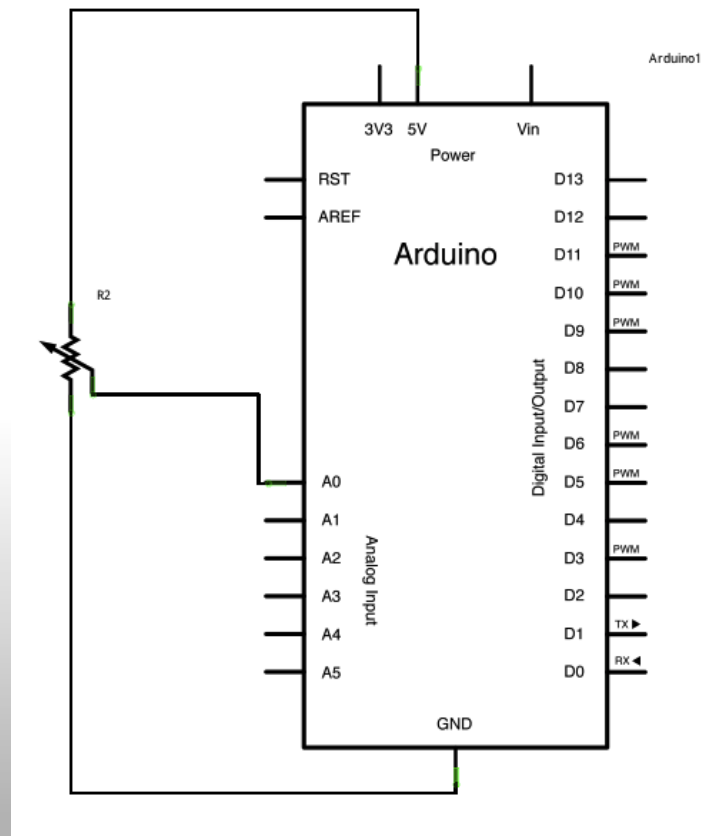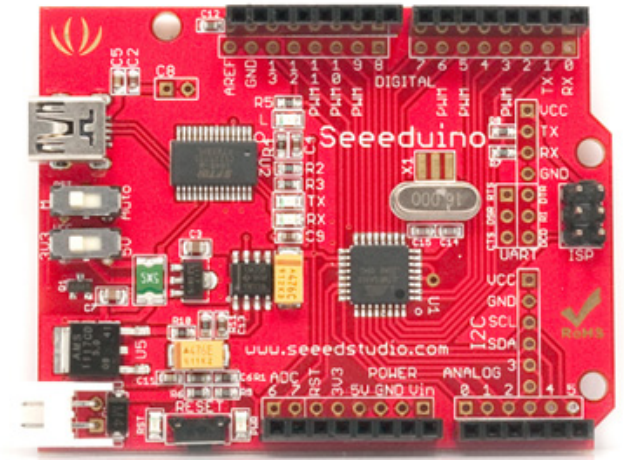- Can read values between 0 and 5V
- 0V -> 0
- 5V -> 1023
- No current flows in



Servo

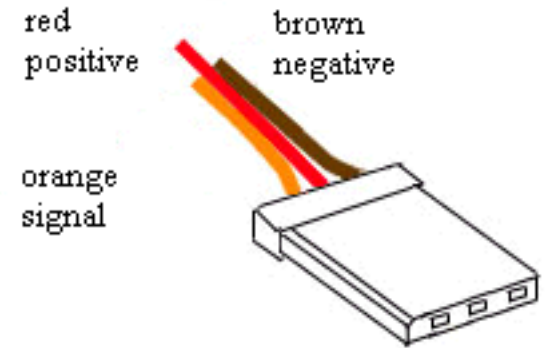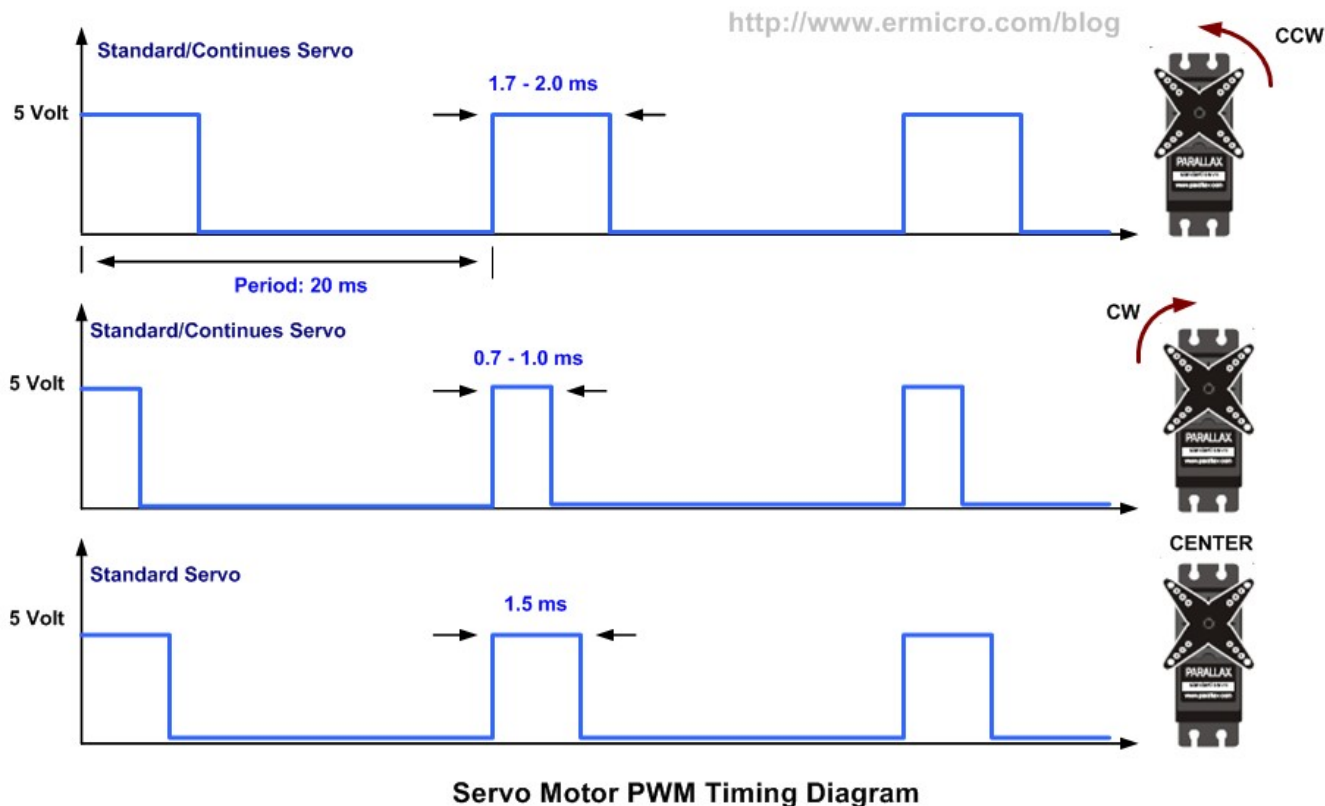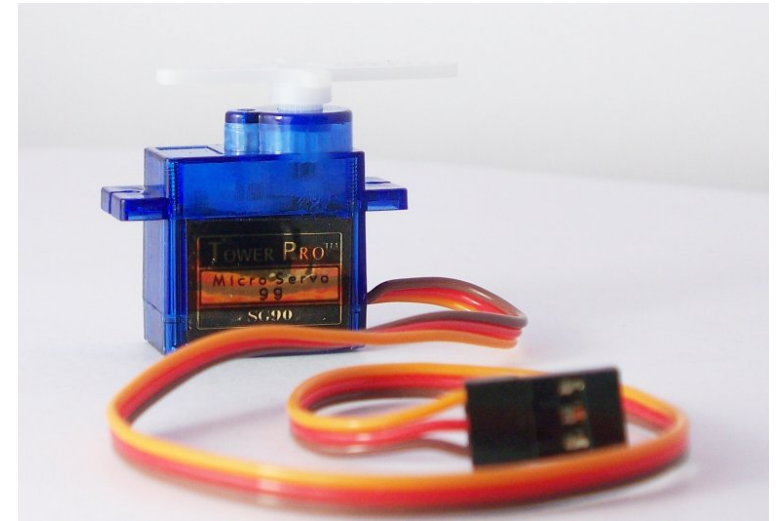- Position controlled motor
- $0^\circ \rightarrow 180^\circ$




Practice



- Drive Servo with potentiometer
- <http://arduino.cc/en/Tutorial/Knob>

Sensors (Variable Resistance)

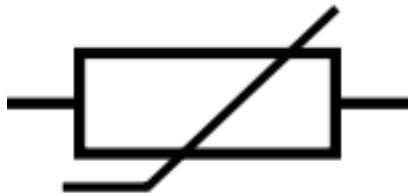- Thermistor (Resistance varies with temperature)



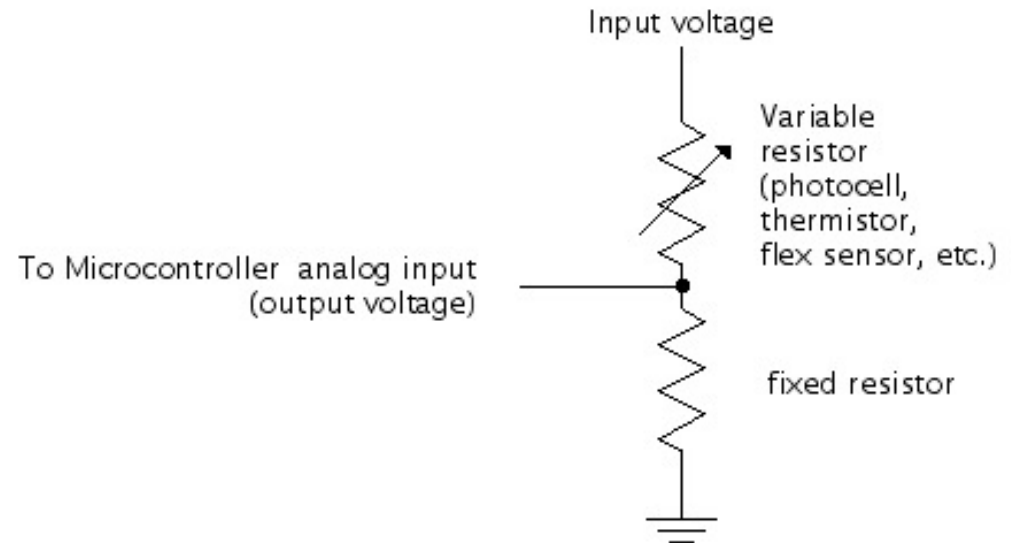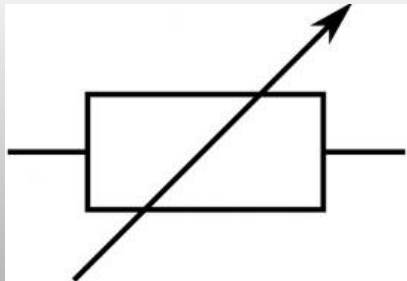- LDR Light Dependent Resistor (Come on!)



Practice

- Drive the servo with one of your resistor sensor
- Or anything else! Just play with the sensors ;-)